

OPERATING INSTRUCTIONS FOR DETERMINATION OF LOW RESISTANCE BY KELVIN'S DOUBLE BRIDGE

OBJECT:

To determine very low resistance by Kelvin's double bridge.

APPARATUS:

Kelvin's double bridge super sensitive galvanometer, Battery eliminator and copper wire whose resistance is to be found.

THEORY:

Let Y be the unknown and X standard known resistance of same order. R_1 , R_2 , R_3 , R_4 are non inductive resistances of higher values as compared to X, Y.

The Balance is obtained when the points B and D are at the same potential. The current at A divides into I_1 and I_x in arms R_1 and X respectively and I_3 passes through R_3 , Potential drop on AD arm = $I_1 R_1$. The sum of potential drops across X and $R_3 = I_x X + I_3 R_3$

But potential at B and D are the same for no deflection in galvanometer, which implies that –

$$I_1 R_1 = I_x X + I_3 R_3 \dots\dots\dots (1)$$

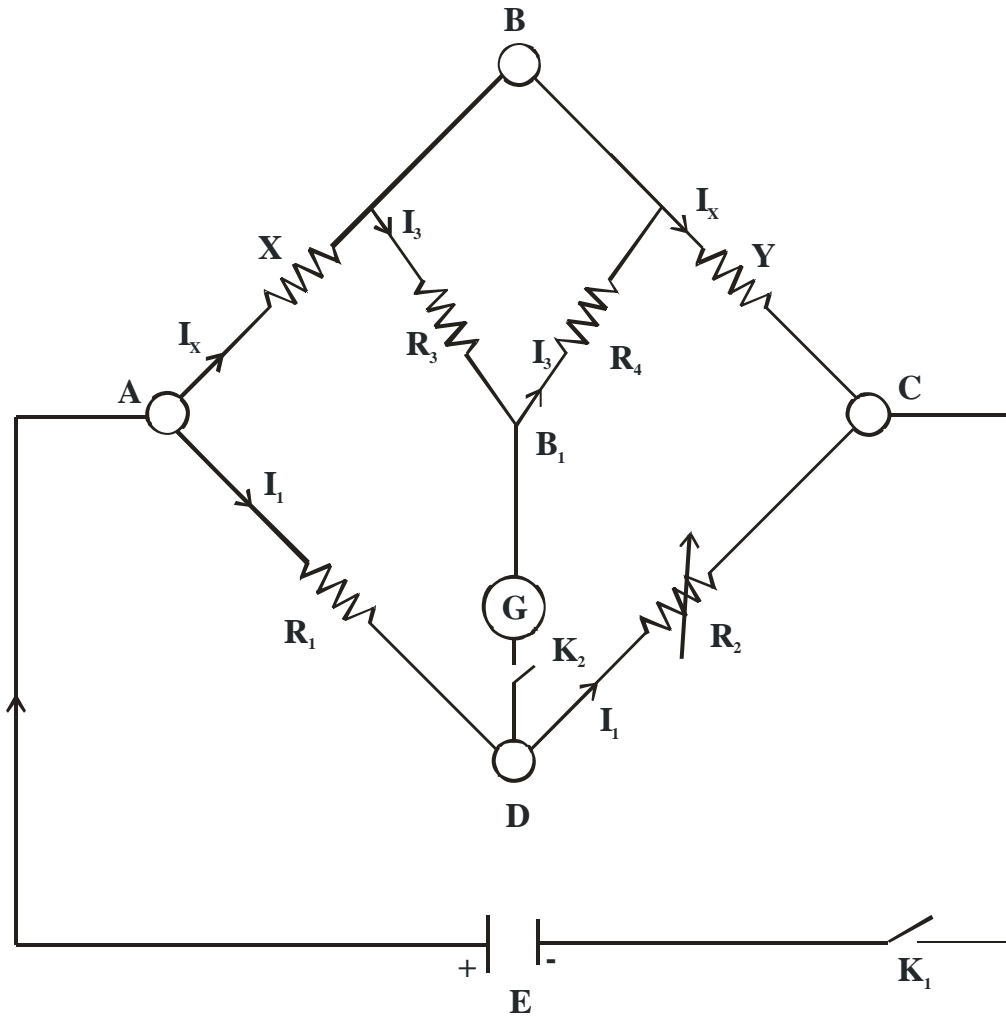


Fig. (1)

Similarly,

P.D. across R₂ = P.D. across R₄ + P.D. across Y

or $I_1 R_2 = I_3 R_4 + I_x Y \dots\dots\dots (2)$

From (1) and (2) we get

$$I_x X = I_1 R_1 - I_3 R_3$$

$$I_x Y = I_1 R_2 - I_3 R_4$$

Dividing

$$\frac{Y}{X} = \frac{I_1 R_2 - I_3 R_4}{I_1 R_1 - I_3 R_3}$$

or

$$\frac{X}{Y} = \frac{R_2 \left[I_1 - I_3 \frac{R_4}{R_2} \right]}{R_1 \left[I_1 - I_3 \frac{R_3}{R_1} \right]}$$

But

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \text{ or } \frac{R_4}{R_2} = \frac{R_3}{R_1} = K$$

$$\therefore \frac{Y}{X} = \frac{R_2 \left[I_1 - I_3 K \right]}{R_1 \left[I_1 - I_3 K \right]}$$

or

$$\frac{Y}{X} = \frac{R_2}{R_1}$$

or

$$\boxed{Y = X \frac{R_2}{R_1}} \dots\dots\dots (3)$$

This equation gives the value of Y in terms of known X, R_1, R_2 resistances.

PROCEDURE:

Refer to Fig. (1) and make connections accordingly.

1. Connect the unknown low resistance in place of Y.
 2. Fix ratio $R_2 : R_1 = 1 : 1$.
 3. Now vary standard resistance X so that on closing battery key K_1 and then galvanometer key K_2 null position in galvanometer is obtained. Calculate unknown resistance using formula (3).
 4. Repeat the experiment with $\frac{R_2}{R_1} = \frac{1}{10}$ and $\frac{R_2}{R_1} = \frac{1}{100}$
-

and find the final mean value of Y.

OBSERVATIONS:

| Ratio $\frac{R_2}{R_1}$ | Value of Standard Resistance X Ohms | $Y = X \frac{R_2}{R_1}$ | Final Value Y Ohm |
|-------------------------|-------------------------------------|-------------------------|-------------------|
| 1 : 1 | | | |
| 1 : 10 | | | |
| 1 : 100 | | | |

RESULT:

The value of unknown low resistance as determined by double Kelvin's bridge is _____ Ohm.

PRECAUTIONS:

1. Galvanometer should be of high sensitivity.
2. Short and thick copper wires should be used for connections if necessary.
3. Battery should supply sufficient current.

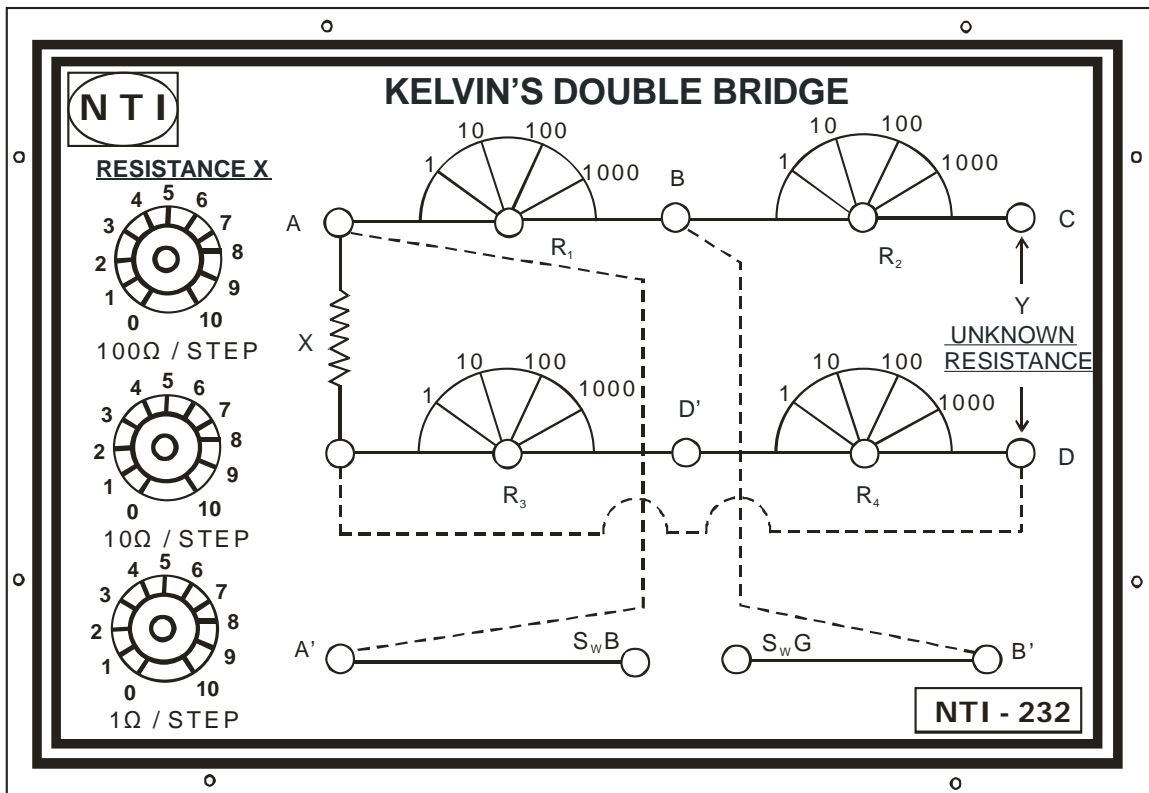


Fig. (2) Panel Diagram

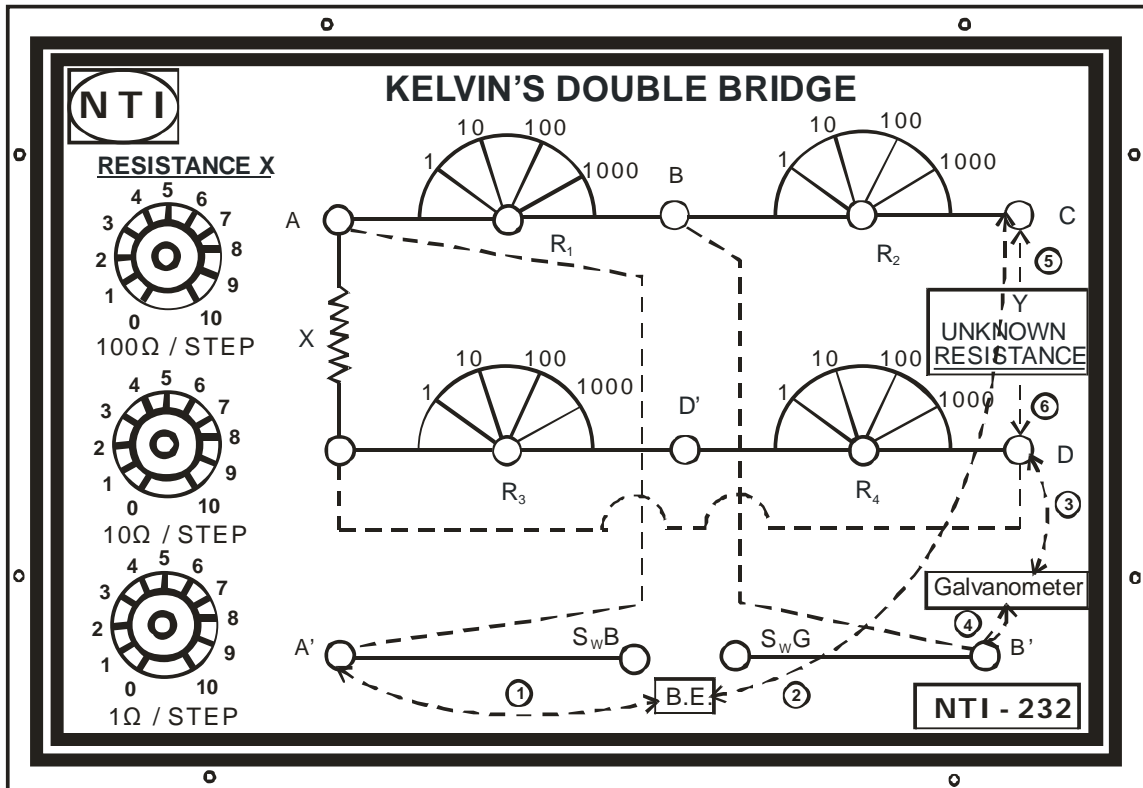


Fig. (3) Connections for Kelvin's Double Bridge
